
#### Drams

- Dynamic RAMS (DRAMs) are cheap and area efficient, but they cannot retain their state indefinitely.
- Information stored in the form of charge on a capacitor can be maintained only for tens of milliseconds.
- Contents must be periodically refreshed.
 
### A single transistor dynamic memory cell




#### A single transistor dynamic memory cell


- Components:
- ▶ 1. Access Transistor: A single transistor acts as a switch to control access to the storage capacitor.
- 2. Storage Capacitor: A capacitor stores the actual data bit in the form of an electrical charge.
- ▶ 3. Bit Line: A bit line is a wire that connects the memory cell to the sense amplifier.
- 4. Word Line: A word line is a wire that selects the memory cell for reading or writing.
 
### 1-Transistor Memory Cell (DRAM)

- Write Operation:
- ▶ 1. Activate the word line.
- 2. Transistor in selected cell is turned ON
- 3.Capacitor gets charged to the voltage supplied to bit line.
- Read Operation:
- ▶ 1. Activate the word line.
- 2. Transistor in selected cell is turned ON
- 3. Cell and bit line share charges
- Capacitor > Threshold voltage, Bit line 1
- Capacitor < Threshold voltage, Bit line 0</p>
- Refresh
   1. Refresh Operation: Since the capacitor's charge leaks over time, the memory
- cell needs to be refreshed periodically by re-writing the stored data.



A single-transistor dynamic memory cell

 

- Address lines are divided into two parts and multiplexed.
- Upper half of address:

Loaded into Row Address Latch using Row Address Strobe (RAS).

Lower half of address:

Loaded into Column Address Latch using Column Address Strobe(CAS).

- A 16-Mbit DRAM chip, configured as 2M X 8 memory organisation
- Cells are organized in the form of array, in rows and columns.
- The cells are organized as 4K X 4K array
- The 4096 cells in each row are divided into 512 groups of 8 cells
- That means a row can store 512 bytes of data
  12 bits to select a row, and 9 bits to select a group (8 bits) in a row. Total of 21 bits.
- Higher order 12 bits-row address and lower order 9 bits column address of a byte
- First apply the row address, RAS signal latches the row address. Then apply the
- . column address, CAS signal latches the address.
- Timing of the memory unit is controlled by a specialized unit which generate RAS and CAS.
- This is asynchronous DRAM

Design 16 M bit DRAM chip (2M X 8 memory organization)

16 2<sup>20</sup>

24 220

**2**<sup>24</sup>

2<sup>12</sup>x 2<sup>12</sup>

Equivalent to 4K x 4K

ROWS=212=4096

**COLUMNS=4096/8=512 columns (8 bits)** 


No: of bits required for ROW Add. X=log2 2<sup>12</sup> =12

No: of bits required for COLUMN Add. Y=log2 2° =9

Total address bit n=x(higher order) + y(lower order)

12+9=21 bits

=A20-A9 + A8-A0

 

16-M bits C512 Sensor write Circuit DATA BUS

#### FAST PAGE MODE

- When the DRAM in last slide is accessed, the contents of all 4096 cells in the selected row are sensed, but only 8 bits are placed on the data lines D7-0, as selected by A8-A0.
- Suppose if we want to access the consecutive bytes in the selected row. This can be done without having to reselect the row.
- Add a latch at the output of the sense circuits in each row.
- All the latches are loaded when the row is selected.
- Consecutive bytes can be transferred by applying consecutive column addresses under the control of successive CAS signals..
- ▶ This allows a block of data to be transferred at a much faster rate than random accesses.
- A small collection/group of bytes is usually referred to as a block. This transfer capability is referred
  to as the FAST PAGE MODE ACCESS
- Good for bulk transfer

The work